

ME 4555 - Lecture 5 - RLC circuits

①

We will cover RLC circuits, op-amps, motors.


This lesson

Common circuit elements


Resistor:  (R) in Ohms (Ω)


Inductor:  (L) in Henrys (H)

Capacitor:  (C) in Farads (F)

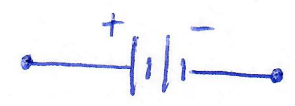Voltage source:  (battery)

 (general)

 (ground)


Current source: 

[indicates voltage reference of 0 volts]

Voltage is like "potential energy" in the sense that it is always measured with respect to a reference. Voltage is either a difference between two points or the value of a single point if measured relative to ground.

Current flows from higher voltage to lower voltage.

Resistors :

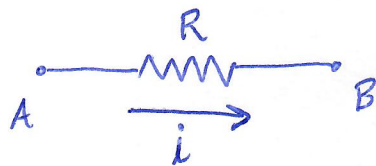


$$i = \frac{1}{R} (V_A - V_B)$$

current flowing through the resistor

voltage difference, a.k.a. "potential difference" between both terminals.
If $V_A > V_B$, current flows right.

Resistors are dissipative elements (energy is lost as heat).

Capacitors :

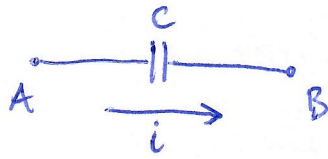


$$i(t) = C \frac{d}{dt} (V_A(t) - V_B(t))$$

current stops flowing once the voltage difference between the terminals becomes constant.

An ideal capacitor stores energy, like a battery.

Inductors :

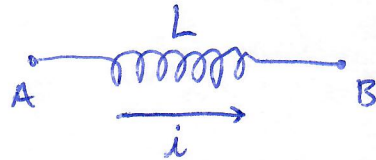

$$V_A(t) - V_B(t) = L \frac{d}{dt} i(t)$$


if current flowing is constant, there is no change in voltage (behaves like a short circuit)

An ideal inductor stores energy in a magnetic field.

★ the capacitor formula is often written in "integral form" as:

$$V_A(t) - V_B(t) = \frac{1}{C} \int i(t) dt.$$


RLC circuit

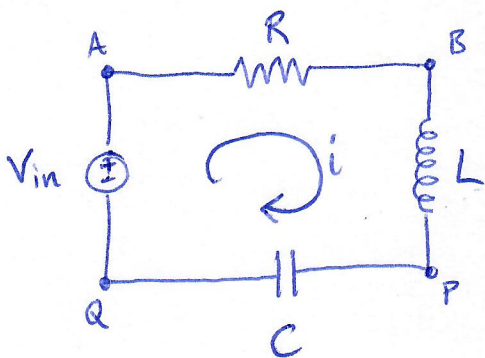

Current flows clockwise because it flows from "+" terminal of voltage source to "-" terminal.

V_{in} refers to the difference in voltage between A and Q, i.e. $V_A - V_Q = V_{in}$.

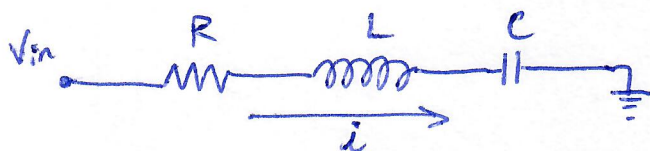We can set, for example, $V_Q = 0$ and then measure all other voltages with respect to this reference, i.e. $V_A = V_{in}$, etc. In this case, an equivalent diagram would be:



Elements are in series, so $i(t)$ is the same for all three elements.

We have, from the definitions on the prev. page:

$$V_A - V_B = iR.$$

$$V_B - V_P = L \frac{di}{dt}$$

$$+ \quad V_P - V_Q = \frac{1}{C} \int i dt$$

$$V_{in} = V_A - V_Q$$

} Sum them together

$$V_{in} = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt$$

This is like an EOM. It shows how changing $V_{in}(t)$ is related to the current $i(t)$ through the circuit.

RLC, cont'd

(4)

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = V_{in} \quad (1)$$

Current is the rate of change of charge: $i(t) = \frac{d}{dt} q(t)$.

Substituting this into (1), we obtain:

$$L \ddot{q} + R \dot{q} + \frac{1}{C} q = V_{in}$$

Compare this to a spring-mass-damper EOM:

$$m \ddot{x} + b \dot{x} + kx = f$$

Note that $R \leftrightarrow b$ is the damping (energy dissipation) term whereas L and C are analogous to m and $\frac{1}{k}$.

Another interpretation: if V_{in} is constant, i.e. $\frac{d}{dt} V_{in} = 0$,

then we can differentiate (1) w.r.t. t and obtain:

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$


Again, same as spring-mass-damper system

Two important rules governing circuits :

5

Kirchoff's current law (KCL)

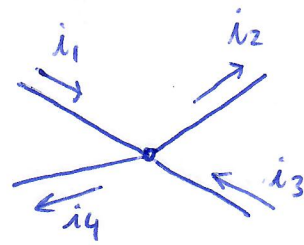
The sum of currents at every junction is equal to zero.



$$i_1 + i_3 = i_2 + i_4$$

Kirchoff's voltage law (KVL)

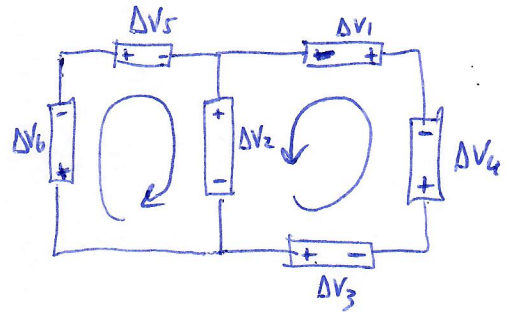
The sum of voltage differences ΔV across any loop is zero.



$$\begin{cases} \Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0 \\ \Delta V_6 + \Delta V_5 + \Delta V_2 = 0 \\ \Delta V_6 + \Delta V_5 - \Delta V_1 - \Delta V_4 - \Delta V_3 = 0 \end{cases}$$


Writing out KCL for each junction and KVL for each loop provides all information available in the circuit.

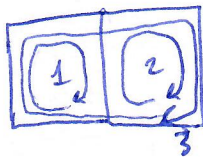Note : for KVL, only need to count loops that involve each path at most twice. e.g.



there are 3 loops here, but only 2 of them are needed (see in example above; third KVL eqn is redundant and follows from the first two).

Ex:

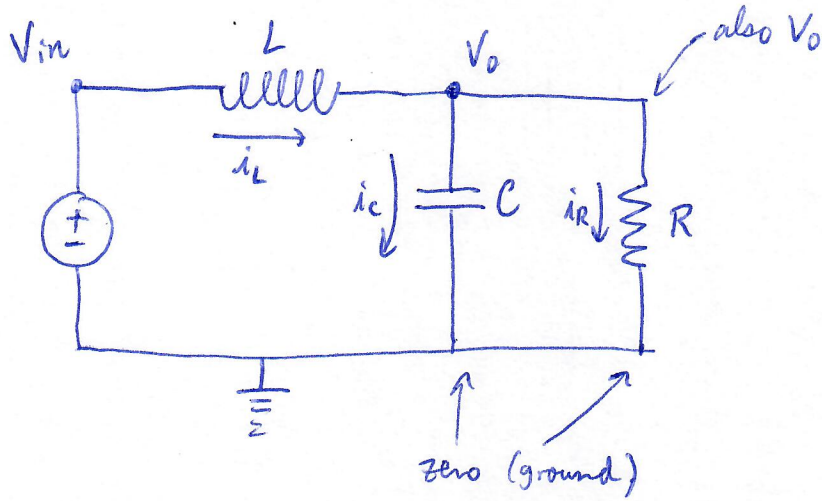

6

Question: how is the output voltage V_o related to the input voltage V_{in} ?

inductor: $V_{in} - V_o = L \frac{di_L}{dt}$ (1)

capacitor: $V_o = \frac{1}{C} \int i_C dt.$ (2)

resistor: $V_o = R i_R$ (3)

KCL @ V_o : $i_L = i_C + i_R$ (4)

Substitute (1), (2), (3) into (4): (to eliminate i_L, i_C, i_R)

$$\underbrace{\frac{1}{L} \int (V_{in} - V_o) dt}_{i_L} = \underbrace{C \dot{V}_o}_{i_C} + \underbrace{\frac{1}{R} V_o}_{i_R}.$$

Differentiate both sides:

$$\frac{1}{L} (V_{in} - V_o) = C \ddot{V}_o + \frac{1}{R} \dot{V}_o$$

Re-arrange:

$$LC \ddot{V}_o + \frac{L}{R} \dot{V}_o + V_o = V_{in}$$

Again, this looks like a spring-mass-damper system, but slightly different than the series RLC circuit from p.3-5.