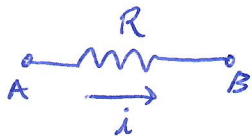



# ME 4555 - Lecture 6 - Op-Amps

(1)


Reminder:



$$V_A - V_B = iR$$

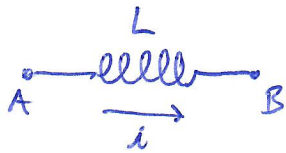


$$V_A - V_B = L \frac{di}{dt}$$

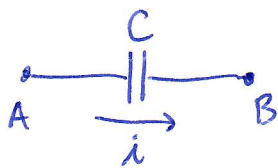

$$V_A - V_B = \frac{1}{C} \int i dt$$

passive elements.  
ideal inductor and capacitor are conservative whereas resistors are dissipative.

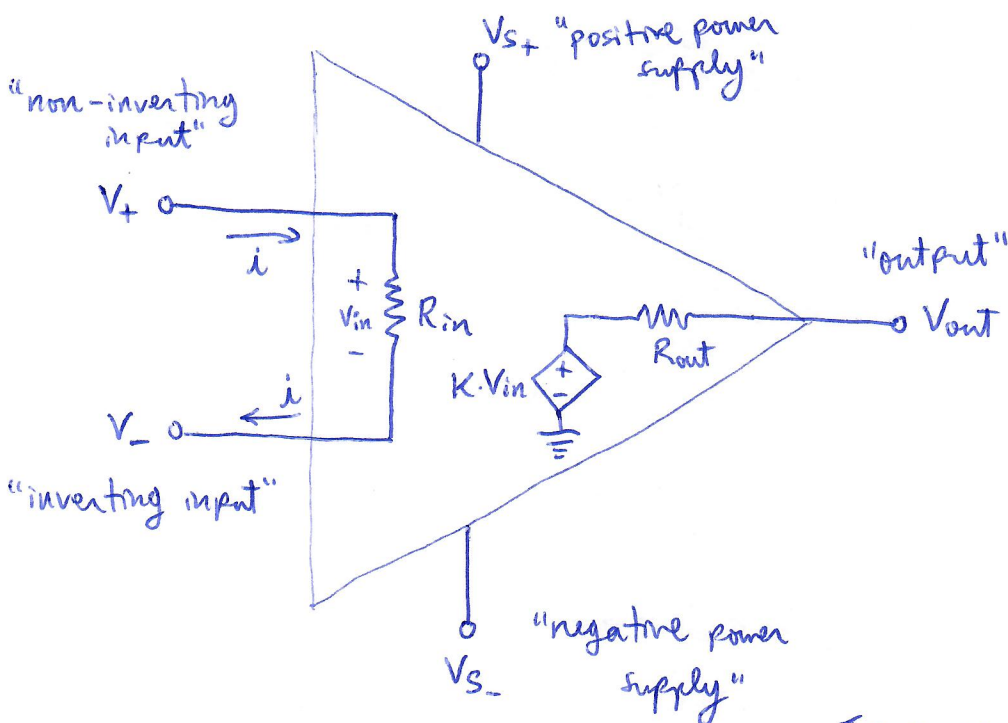Today, we'll introduce operational amplifiers (opamps). Opamps are active elements (they can add energy to the system). Somewhat realistic model of an opamp:



Because of  $R_{in}$ :

$$V_{in} = V_+ - V_-$$

$$V_{in} = i R_{in}$$

typically very large, so  $i \approx 0$ .

Because of voltage source,

$$V_{out} = K \cdot V_{in}$$

typically very large,  $K \approx 10^6$

$R_{out}$  is typically small.

In a real opamp, the output is

bounded by the supply. So


$$V_c \leq V_{out} < V_c$$

In an ideal opamp,  $R_{in} = \infty$ ,  $K = \infty$ ,  $R_{out} = 0$ ,

$V_{S+} = +\infty$ ,  $V_{S-} = -\infty$ . Therefore,  $i = 0$  and  $V_+ = V_-$


Note:  $V_{out}$  is not generally zero.

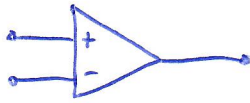We usually represent an ideal opamp with the symbol:



Note: the "+" and "-" terminals are important! Sometimes we will flip the diagram to avoid crossed wires, so be mindful of the labels!

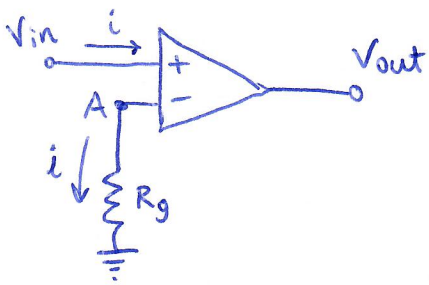Simple opamp circuit without feedback (open-loop): ("comparator")



$$\text{since } \begin{cases} V_{out} = K \cdot (V_{in} - V_A) \\ V_A = i R_g, \quad V_{in} - V_A = i R_{in} \end{cases}$$

$K$  and  $R_{in}$  are the internal gain and input resistance of the opamp.

i) solve for  $V_A$  and eliminate  $i$  from last two equations:

$$V_A = i R_g = \frac{R_g}{R_{in}} (V_{in} - V_A) \Rightarrow V_A = \frac{R_g}{R_{in} + R_g} V_{in}$$

ii) substitute into first equation:

$$V_{out} = K (V_{in} - V_A) = \frac{K}{1 + \frac{R_g}{R_{in}}} V_{in}$$

→ goes to  $+\infty$  as  $K \rightarrow \infty$  and  $R_{in} \rightarrow \infty$ .  
for an "ideal" opamp, the output would be  $\pm\infty$ . Here, we observe saturation:


In reality (since we can't have infinite voltages), the "ideal opamp" assumption can't be used. We observe instead:

$$V_{out} = \begin{cases} V_{S+} & \text{if } V_{in} > 0 \\ V_{S-} & \text{if } V_{in} < 0 \end{cases}$$
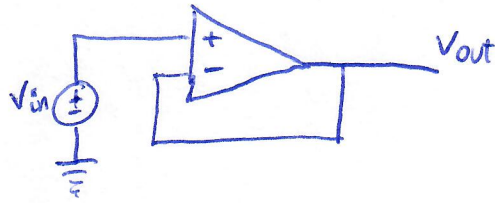
# Negative vs Positive Feedback

3

negative feedback uses the  
"-" input for feedback:




$$\text{we have } V_{out} = K(V_{in} - V_{out}) \Rightarrow V_{out} = \frac{K}{1+K} V_{in}$$

$$\text{as } K \rightarrow \infty, \boxed{V_{out} = V_{in}}$$

positive feedback uses the

"+" input for feedback:

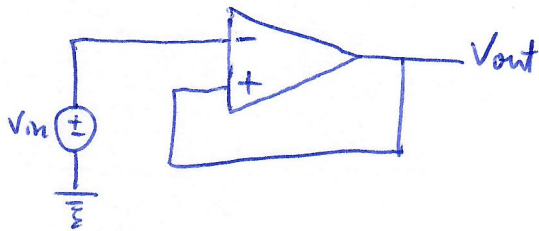

this is  
incorrect!!



$$\text{We have } V_{out} = K(V_{out} - V_{in}) \Rightarrow V_{out} = \frac{K}{K-1} V_{in}$$

$$\text{as } K \rightarrow \infty, \boxed{V_{out} = V_{in}}$$


What's the problem? in negative feedback, the opamp works to keep  $V_{in} = V_{out}$ . If  $V_{in}$  increases slightly so  $V_{+} > V_{-}$ ,  $V_{out}$  (i.e.  $V_{-}$ ) will increase to restore the balance. Likewise if  $V_{+} < V_{-}$ ,  $V_{out}$  will decrease to restore the balance.

In positive feedback, small errors are amplified instead of attenuated. So such circuits are unstable and will cause saturation and the opamp will cease to behave ideally.

Analogy :

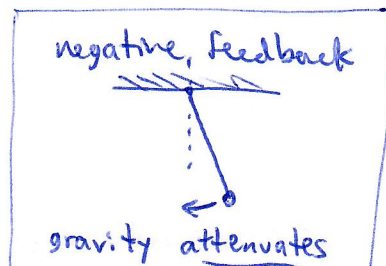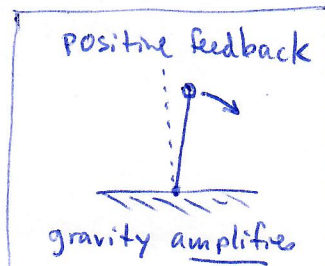

Ex: non-inverting amplifier

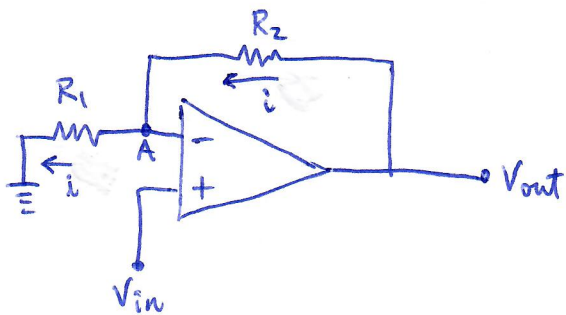

ideal opamp: \* voltage input equal:  $V_{in} = V_A$ .  
 \* zero input current so both  $i$ 's are same.

voltage drop across resistors:

$$V_A = iR_1, \quad V_{out} - V_A = iR_2.$$


i) Eliminating  $i$ , we get:  $V_{out} - V_A = iR_2 = V_A \cdot \frac{R_2}{R_1}$

ii) Substitute  $V_A = V_{in}$ :  $V_{out} - V_{in} = \frac{R_2}{R_1} V_{in}$

iii) Solve for  $V_{out}$ :  $V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$

← can tune  $R_1, R_2$  to change how much output is amplified!

Ex: inverting amplifier

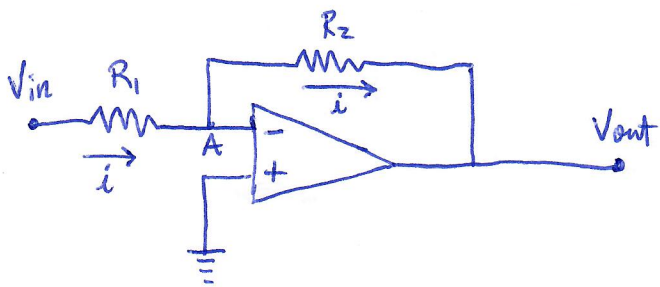

ideal opamp: \*  $V_A = 0$   
 \* both  $i$ 's are the same.

voltage drop across resistors:


$$V_{in} - V_A = iR_1, \quad V_A - V_{out} = iR_2.$$

setting  $V_A = 0$  and solving for  $V_{out}$  (eliminate  $i$ ), we obtain:

$$V_{in} = iR_1, \quad V_{out} = -iR_2 \Rightarrow V_{out} = -\frac{R_2}{R_1} V_{in}$$

Ex

(5)

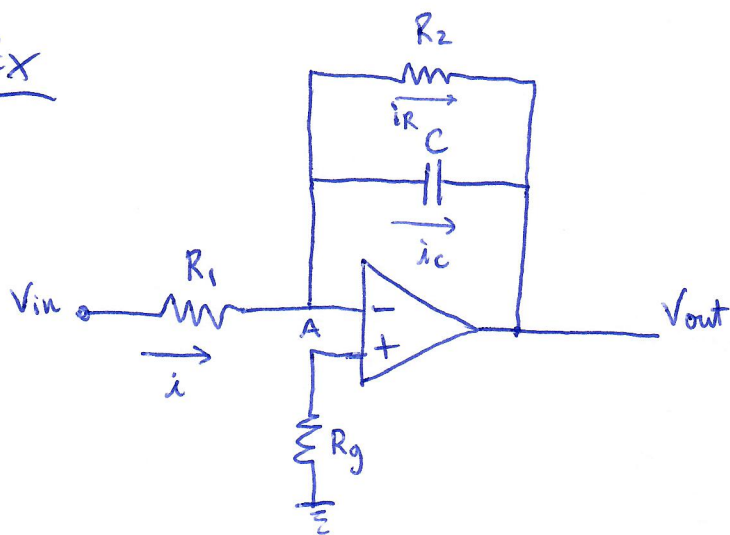

What is  $V_{out}$  in terms of  $V_{in}$ ? (ideal opamp)

\* current into opamp input is zero, so by KCL:  $i = i_c + i_R$ .

\* input voltages is the same so

$$V_A = 0.$$

For  $R_1$ :  $V_{in} = i R_1$

For  $R_2$ :  $-V_{out} = i_R R_2$

For  $C$ :  $i_c = -C \dot{V}_{out}$

KCL  $\rightarrow$

$$\underbrace{\frac{V_{in}}{R_1}}_i = \underbrace{-C \dot{V}_{out}}_{i_c} + \underbrace{-\frac{V_{out}}{R_2}}_{i_R}$$

$$\Rightarrow \boxed{C \dot{V}_{out} + \frac{1}{R_2} V_{out} = -\frac{1}{R_1} V_{in}}$$

if we make  $R_2 \rightarrow \infty$  (i.e. make an open circuit; remove  $R_2$  entirely)

we obtain  $C \dot{V}_{out} = -\frac{1}{R_1} V_{in}$

$$\Rightarrow \boxed{V_{out} = -\frac{1}{R_1 C} \int V_{in}(t) dt.}$$

this is one way to construct an integrator!