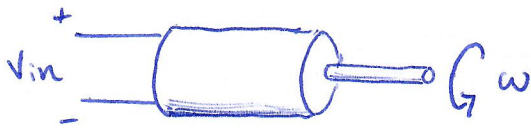


ME 4555 - Lecture 7 - DC motors


(1)




Voltage supply causes shaft to spin ($\omega = \dot{\theta}$ is angular speed of shaft)

Three fundamental principles (Lorentz's force law + Faraday's laws of induction):

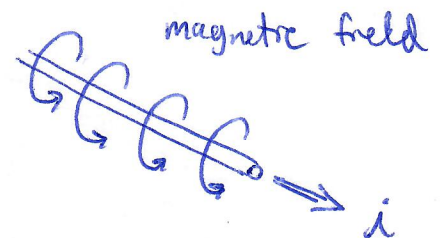
1) A current in a wire establishes a magnetic field around the wire;



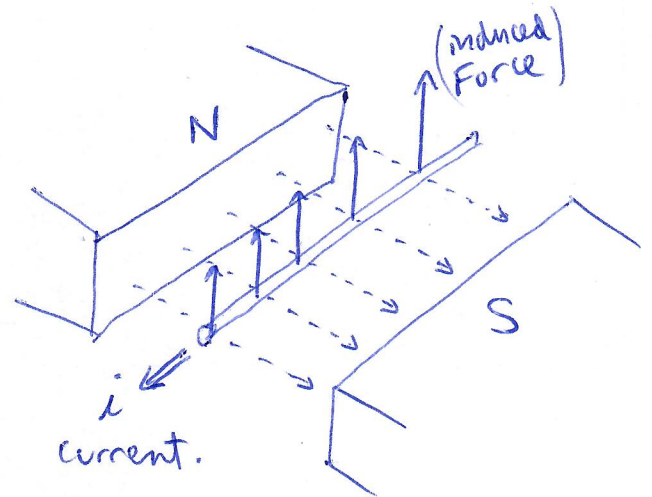
2) A current-carrying wire in a magnetic field has a force on it (perpendicular to the wire + field) and proportional to current: $F \propto i$



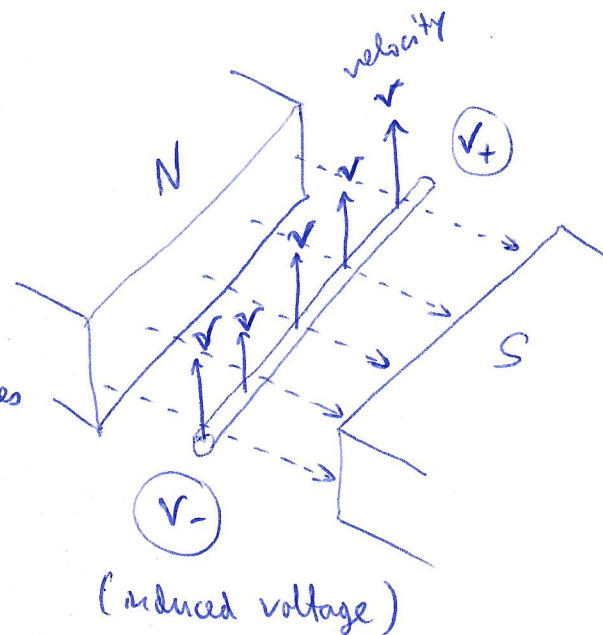3) A wire moving in a magnetic field will induce a voltage between the ends of the wire. The wire becomes like a voltage source whose voltage opposes the current from step 2 that might cause a force that would produce this velocity in the wire.





Basic idea of a motor:
angular speed ω

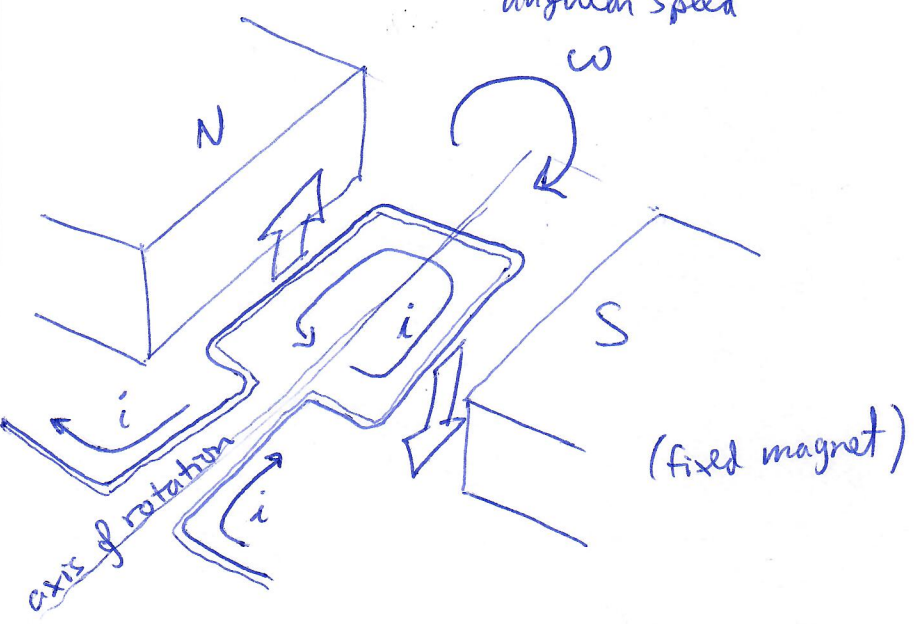

- A loop of wire sits in a fixed magnetic field (from fixed magnet)
- Current pushed through wire causes forces on the loop, makes it spin.

Model circuit:

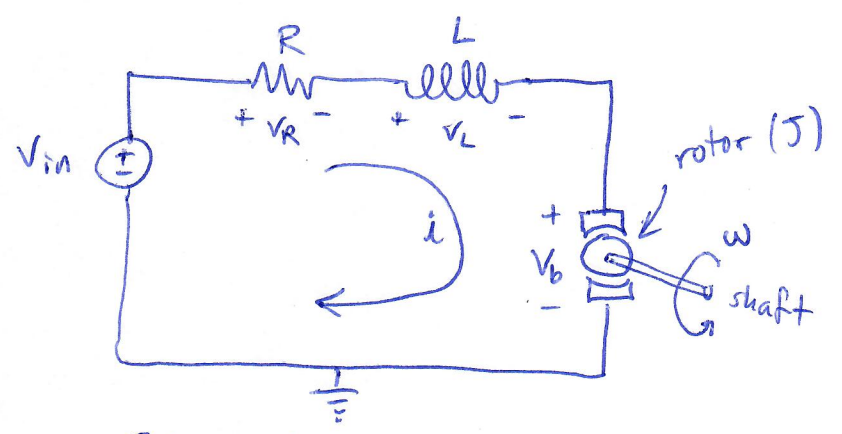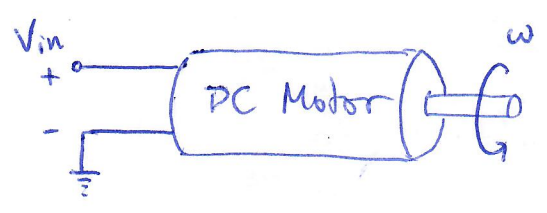


R models the loss in the long wire (resistive (heat losses))

L models the coil effect acting like an inductor.

V_b is the voltage produced by the motor spinning that opposes the current. Also called "back emf".

CAUSAL CHAIN:

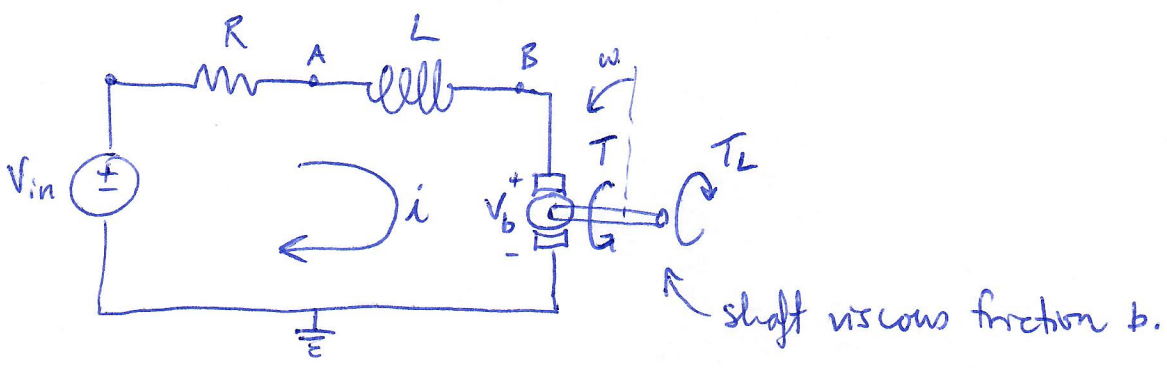- ★ From law #2, current induces a force (torque) in the shaft.
 - ↓
 - ★ From mechanics EOM, torque in shaft induces rotation (Newton's 2nd law).
 - ↓
 - ★ From rotation motion (law #3), voltage V_b is induced that opposes original current.
- { this continues until balance is achieved?



Electrical part :


$$V_{in} - V_A = iR$$

$$V_A - V_B = L \frac{di}{dt}$$

KVL :

$$L \frac{di}{dt} + Ri + V_b = V_{in}$$

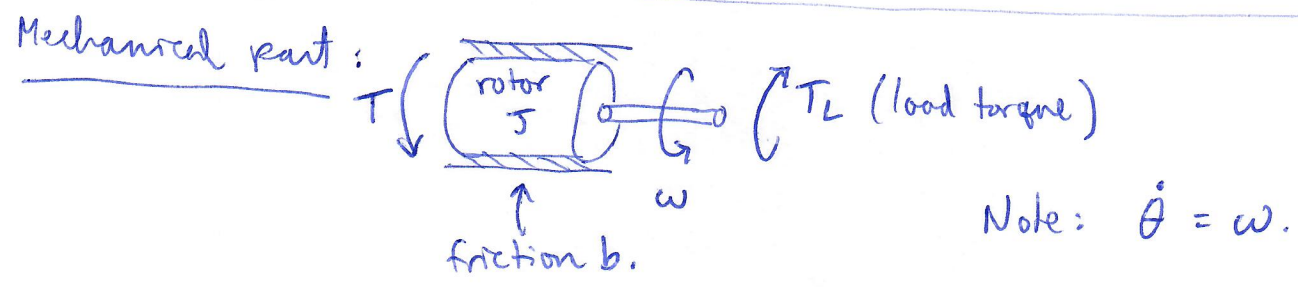Electrical → mechanical : $T = K_m i$ where K_m is the "motor-torque constant" (supplied by the motor manufacturer). Units of K_m are $\left[\frac{N \cdot m}{A} \right]$.



EOM :

$$J\dot{\omega} = T - \underbrace{T_L}_{\text{load}} - \underbrace{b\omega}_{\text{friction}}$$

mechanical → electrical : $V_b = K_b \cdot \omega$ where K_b is the "back-emf constant" (supplied by the manufacturer) Units of K_b are $\left[\frac{\text{Volts}}{\text{rad/sec}} \right]$ or more commonly $\left[\frac{\text{Volts}}{\text{rpm}} \right]$.

Note: If using SI units, $K_m = K_b$. This is because power is conserved. So (mechanical power) = (electrical power)

$$\Rightarrow P = \underbrace{T\omega}_{\text{mechanical}} = \underbrace{V_b i}_{\text{electrical}}$$

But $T = K_m i$ and $V_b = K_b \omega$.

so $P = K_m i \omega = K_b i \omega \Rightarrow \boxed{K_m = K_b}$

Note: must use SI units!
 i.e. $\left[\frac{\text{N}\cdot\text{m}}{\text{A}}\right]$ for K_m and $\left[\frac{\text{Volt}\cdot\text{sec}}{\text{rad}}\right]$ for K_b

All equations for the motor:

$$\left\{ \begin{array}{l} L \frac{di}{dt} + Ri + V_b = V_{in} \\ T = K_m i \\ J\dot{\omega} = T - T_L - b\omega \\ V_b = K_b \omega \end{array} \right\} \Rightarrow \boxed{\left\{ \begin{array}{l} L \frac{di}{dt} + Ri + K_b \omega = V_{in} \\ J\dot{\omega} + b\omega - K_m i = -T_L \end{array} \right.}$$

It's possible to eliminate i and get a single equation for ω .

Solve for i in 2nd eqn: $i = \left(\frac{J\dot{\omega} + b\omega + T_L}{K_m} \right)$.

Substitute into 1st eqn:

$$L \left(\frac{J\ddot{\omega} + b\dot{\omega} + \dot{T}_L}{K_m} \right) + R \left(\frac{J\dot{\omega} + b\omega + T_L}{K_m} \right) + K_b \omega = V_{in}$$

$$\Rightarrow \boxed{\frac{LJ}{K_m} \ddot{\omega} + \left(\frac{RJ + Lb}{K_m} \right) \dot{\omega} + \left(\frac{Rb}{K_m} + K_b \right) \omega = \underbrace{\left(V_{in} - \frac{L}{K_m} \dot{T}_L - \frac{R}{K_m} T_L \right)}_{\text{external inputs (Torques, voltages)}}$$

For an ideal motor, we often assume $L=0$, $b=0$ (frictionless)

$$\Rightarrow \boxed{\frac{RJ}{K_m} \dot{\omega} + K_b \omega = V_{in} - \frac{R}{K_m} T_L}$$

Chain of causality for DC motor.

5

Initially, $\omega = 0$ (no motion), no voltage or current.

- connect the battery, i.e. $V_{in} > 0$.
- V_{in} causes current to flow through the windings.
- - Flowing current generates torque on shaft ($T = K_m i$)
- Torque on shaft causes acceleration due to $\Sigma T_{ext} = J \ddot{\omega}$
- ω (angular speed) increases as direct result of acceleration.
- motion of coil causes back-emf: $V_b = K_b \omega$.
- V_b causes reduction in current entering the coil

Ultimately, balance is achieved and the motor spins at a constant speed. To find this speed, set $\dot{\omega} = \ddot{\omega} = 0$ in the differential equation:

$$\left(\frac{R_b}{K_m} + K_b\right) \omega = \left(V_{in} - \frac{R}{K_m} T_L\right)$$

$$\Rightarrow \omega = \frac{V_{in} - \frac{R}{K_m} T_L}{\frac{R_b}{K_m} + K_b}$$



Future: larger V_{in} \rightarrow faster ω .
larger T_L \rightarrow slower ω .
larger b \rightarrow slower ω

Interesting:

- ★ J doesn't matter!
Affects rate of change of speed $\dot{\omega}$ (acceleration) but not final speed.
- ★ Same with L ; doesn't affect final speed.

Bonus : motors in reverse : generators!


6

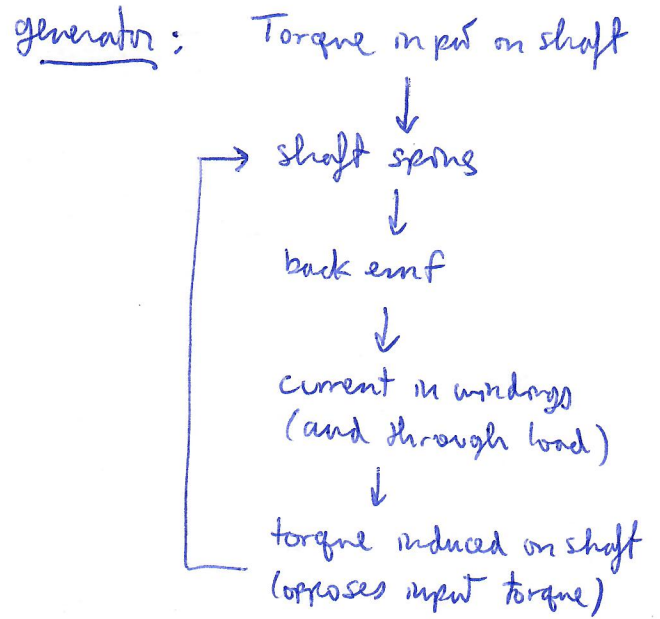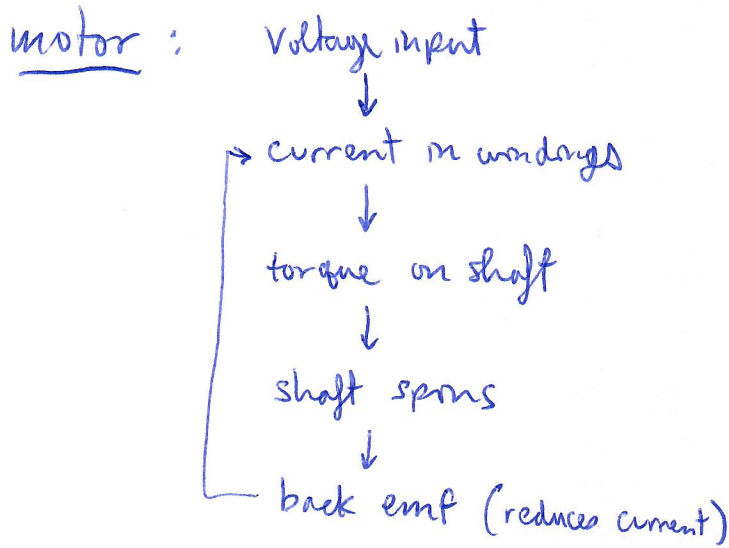

The equations for a generator are the same as for a motor!

{let's keep the same sign conventions}

same equations as for motor:

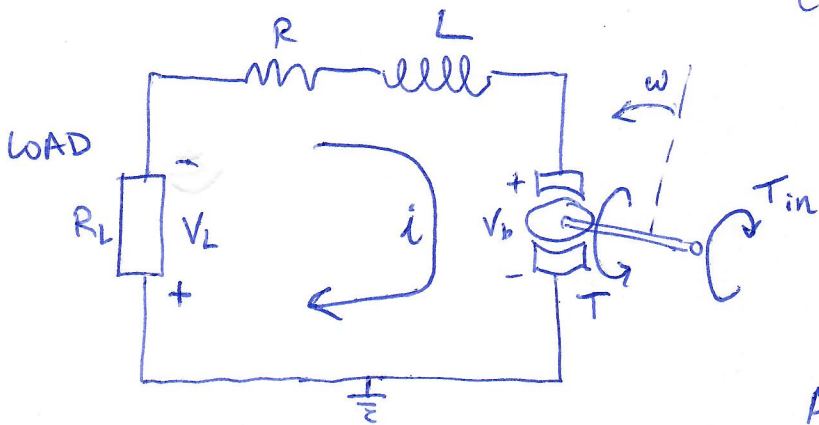

$$\begin{cases} L \frac{di}{dt} + Ri + K_b \omega = -V_L \\ J\dot{\omega} + b\omega - K_m i = -T_{in} \end{cases}$$

Assume load is R_L . So $V_L = iR_L$.

For a generator, we typically care about the current driven through the load. So we can eliminate ω instead. After some algebra...

$$\left(\frac{JL}{K_b}\right) \frac{d^2 i}{dt^2} + \left(\frac{J(R+R_L) + Lb}{K_b}\right) \frac{di}{dt} + \left(\frac{b(R+R_L)}{K_b} + K_m\right) i = T_{in}$$

So steady-state current through load is:

$$i_{ss} = \frac{T_{in}}{\frac{b(R+R_L)}{K_b} + K_m}$$