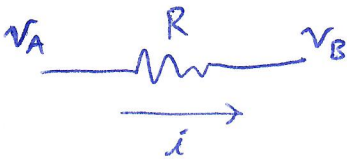

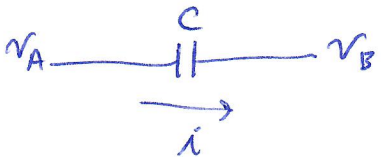


ME 4555 - Lecture 13 - Circuit analysis using TFs

(1)

Circuits are often easier to analyze in the s-domain instead of the time domain. This simply means that we look at $V(s), I(s)$ instead of $v(t), i(t)$.

	<u>time domain</u>	<u>s-domain</u>
	$v_A - v_B = Ri$	$V_A - V_B = \boxed{R} I$
	$v_A - v_B = L \frac{di}{dt}$	$V_A - V_B = \boxed{Ls} I$
	$v_A - v_B = \frac{1}{C} \int i(t) dt$	$V_A - V_B = \boxed{\frac{1}{Cs}} I$

Each element has formula of the form $V_A - V_B = Z I$ where $Z(s)$ is called the impedance.

$$\left\{ \begin{array}{l} Z_R = R \\ Z_L = Ls \\ Z_C = \frac{1}{Cs} \end{array} \right.$$

Note: $\mathcal{L}\left\{\int i dt\right\} = \frac{1}{s} I$

Equivalently, we could start with

$$v_A - v_B = \frac{1}{C} i \quad \left. \vphantom{v_A - v_B = \frac{1}{C} i} \right\} \mathcal{L}$$


$$s(V_A - V_B) = \frac{1}{C} I$$

$$V_A - V_B = \frac{1}{Cs} I$$

Equivalent impedances


(2)

Series connection:

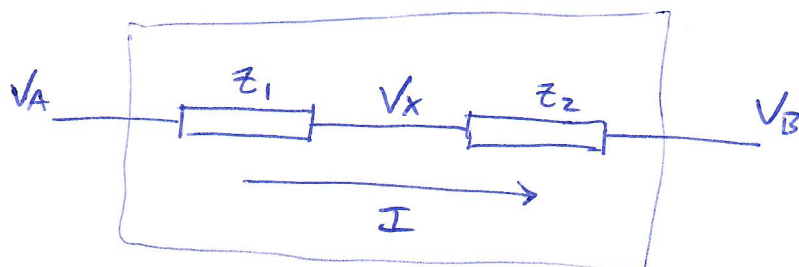


$$\begin{cases} V_A - V_x = Z_1 I \\ V_x - V_B = Z_2 I \end{cases} \Rightarrow V_A - V_B = \underbrace{(Z_1 + Z_2)}_{Z_{eq}} I$$

so this is equivalent to

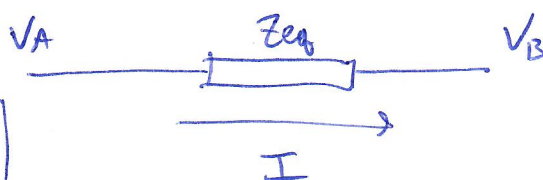

with $Z_{eq} = Z_1 + Z_2$

Parallel connection:

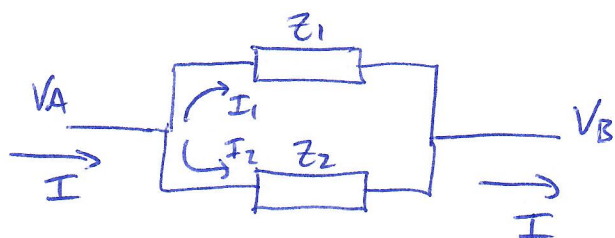


$$\begin{cases} V_A - V_B = Z_1 I_1 \\ V_A - V_B = Z_2 I_2 \\ I_1 + I_2 = I \end{cases} \Rightarrow \underbrace{\frac{V_A - V_B}{Z_1}}_{I_1} + \underbrace{\frac{V_A - V_B}{Z_2}}_{I_2} = I$$

$$\Rightarrow \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) (V_A - V_B) = I$$

$$\Rightarrow V_A - V_B = Z_{eq} I$$



where
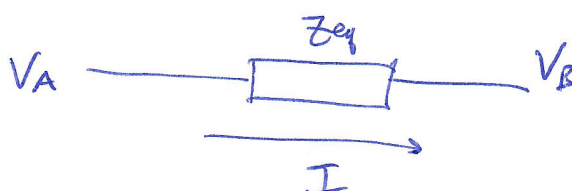
$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$




Ex RLC circuit.

(3)

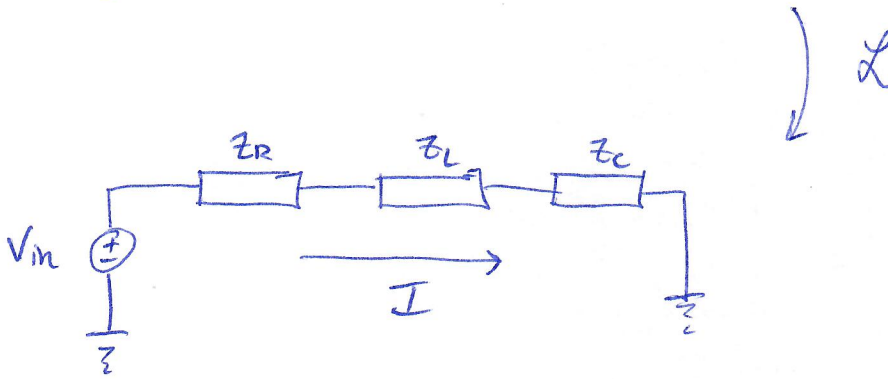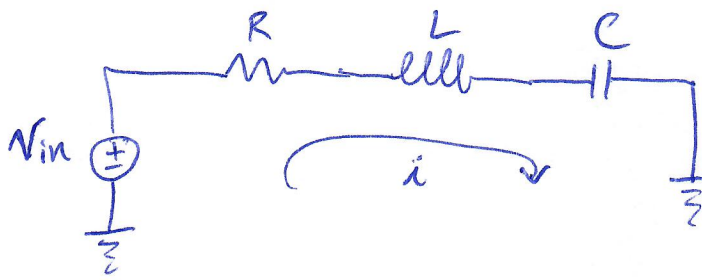

where
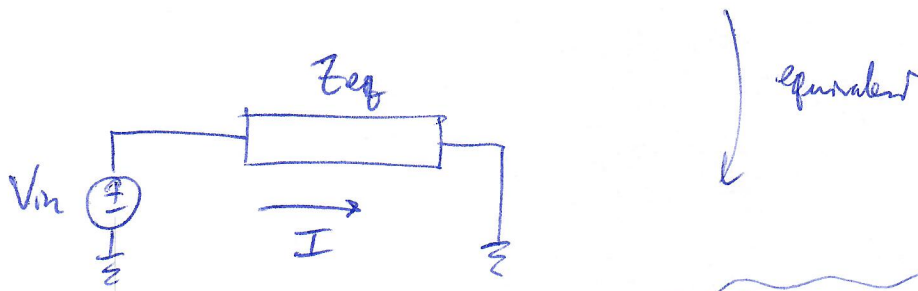
$$\begin{cases} Z_R = R \\ Z_L = Ls \\ Z_C = \frac{1}{Cs} \end{cases}$$



where $Z_{eq} = Z_R + Z_L + Z_C$.

transfer function from $V_{in} \rightarrow I$

$$G(s) = \frac{I}{V_{in}} = \frac{Cs}{LCs^2 + RCs + 1}$$

So $V_{in} = Z_{eq} I$

$\Rightarrow V_{in} = \left(R + Ls + \frac{1}{Cs} \right) I$

$\Rightarrow sV_{in} = \left(Ls^2 + Rs + \frac{1}{C} \right) I$

multiply by s (i.e. differentiate)


$\Rightarrow \dot{V}_{in} = L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C}$

\mathcal{L}^{-1} (inverse Laplace)

or, if we let $Q = \frac{1}{s} I$ ($q(t) = \int i(t) dt$, charge is integral of current)

then $V_{in} = \left(Ls^2 + Rs + \frac{1}{C} \right) Q \Rightarrow V_{in} = L\ddot{q} + R\dot{q} + \frac{1}{C}q$

Ex inverting amplifier (with impedances)

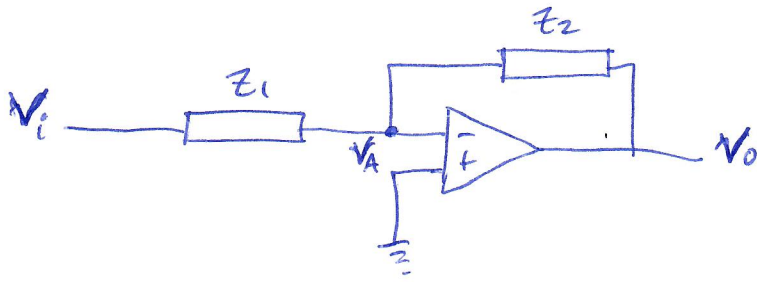

Recall: $V_i - V_A = Z_1 I$


$$V_A - V_o = Z_2 I$$

$$V_A = 0$$

because no current enters the opamp in the $+$ or $-$ terminals and voltages are equal, so since $V_+ = 0$ (ground), $V_- = V_A = 0$ also.

Solving, we find that
$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

Ex inverting amplifier with inductor.

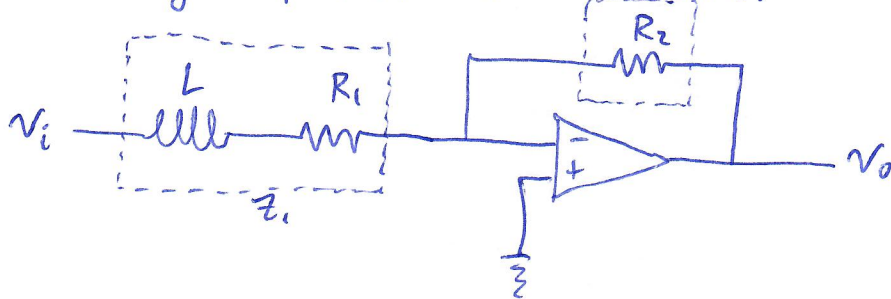

Z_1 is series connection of inductor (L_s) and resistor (R_1).

so $Z_1 = L_s + R_1$, $Z_2 = R_2$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_2}{L_s + R_1}$$


can also obtain ODE:

$$\frac{(L_s + R_1)}{R_2} V_o = -V_i$$

$$\Rightarrow \frac{L}{R_2} \dot{V}_o + \frac{R_1}{R_2} V_o = -V_i$$

Ex cascaded inventory amplifiers.

5

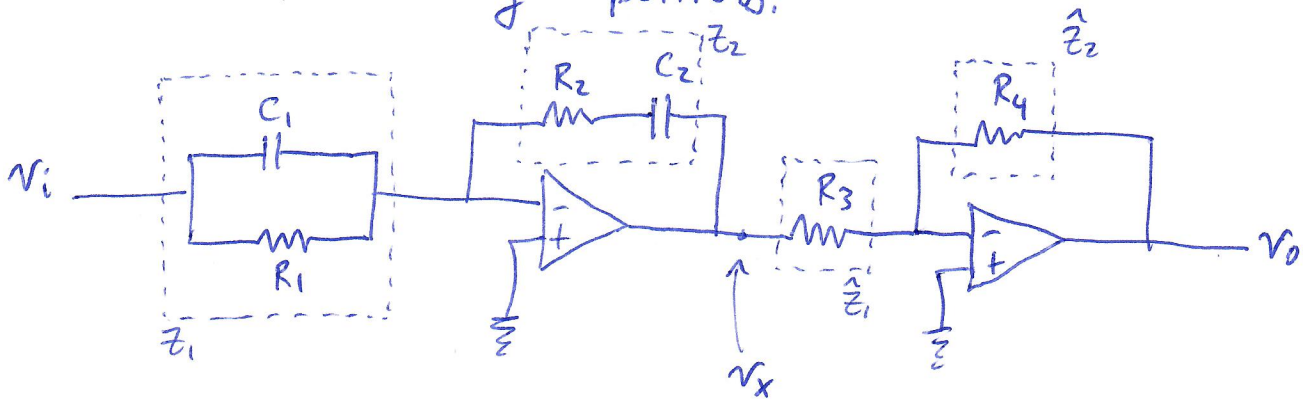

First part (from v_i to v_x):

$$Z_1 \text{ is } C_1 \parallel R_1: \frac{1}{Z_1} = \frac{1}{\left(\frac{1}{Cs}\right)} + \frac{1}{R_1} \Rightarrow \boxed{Z_1 = \frac{R_1}{R_1 C_1 s + 1}}$$

$$Z_2 \text{ is } R_2 + C_2: Z_2 = \frac{1}{\frac{1}{C_2 s} + R_2} \Rightarrow \boxed{Z_2 = \frac{R_2 C_2 s + 1}{C_2 s}}$$

$$\text{therefore: } \frac{v_x}{v_i} = -\frac{Z_2}{Z_1} = -\frac{(R_1 C_1 s + 1)(R_2 C_2 s + 1)}{R_1 C_2 s}$$

Second part (from v_x to v_o):

$$\hat{Z}_1 \text{ is } R_3$$


$$\hat{Z}_2 \text{ is } R_4$$

$$\text{therefore } \frac{v_o}{v_x} = -\frac{\hat{Z}_2}{\hat{Z}_1} = -\frac{R_4}{R_3}$$

$$\text{So } \boxed{\frac{v_o}{v_i} = \left(\frac{v_o}{v_x}\right) \left(\frac{v_x}{v_i}\right) = \frac{R_4 (R_1 C_1 s + 1)(R_2 C_2 s + 1)}{R_3 R_1 C_2 s}}$$

Note: this is one way to implement a PID controller using an analog circuit! (more on this later...)

Ex

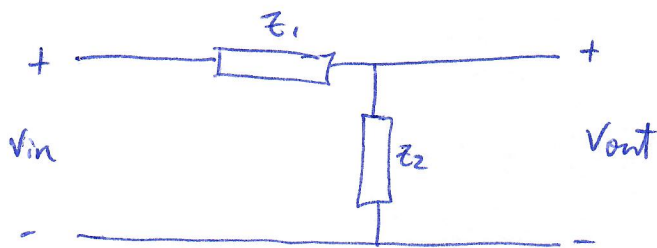


what is the transfer function $\frac{V_{out}}{V_{in}}$?

6

Does this even make sense? there is no "source"! Is there even current?

lets put a source at V_{in} :

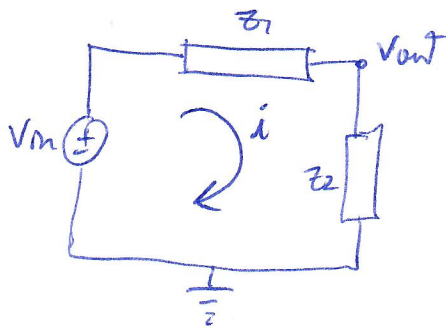


$$\text{then: } \begin{cases} V_{in} - V_{out} = Z_1 I \\ V_{out} = Z_2 I \end{cases}$$

Substitute to eliminate I : $V_{in} - V_{out} = \frac{Z_1}{Z_2} V_{out}$

$$\Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}}$$

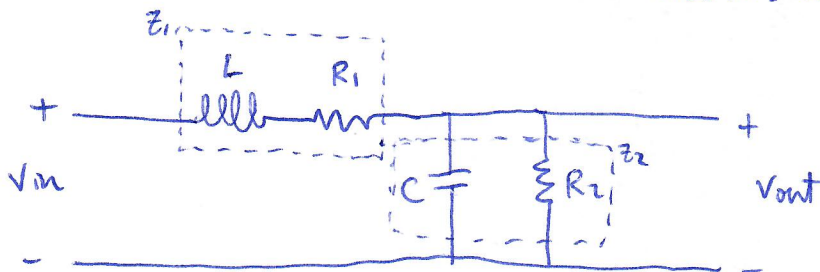Ex: model for an electric transmission line (used in med-range power transmission)



$$Z_1: L + R_1 \rightarrow Z_1 = (Ls + R_1)$$

$$Z_2: C \parallel R_2 \rightarrow \frac{1}{Z_2} = Cs + \frac{1}{R_2} \Rightarrow Z_2 = \frac{R_2}{R_2Cs + 1}$$

Using same result from previous example:

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{R_2}{R_2Cs + 1}}{Ls + R_1 + \frac{R_2}{R_2Cs + 1}} = \boxed{\frac{R_2}{(Ls + R_1)(R_2Cs + 1) + R_2}}$$